

Objective / Aim of the Experiment

To measure the value of high resistance by substitution method

Apparatus Required

Given high resistance
DC Power Supply
Galvanometer
High resistance boxes
One way key
Two way key
Connecting wires

Formula Used

$$X = \left[\frac{R(G+S)}{S} + G \right] \frac{\theta_2}{\theta_1} - G$$


Where, G = Resistance of galvanometer

S = resistance of Shunt

R = high resistance

θ_1, θ_2 = Deflection with X and R, S

Circuit Diagram for Substitution Method

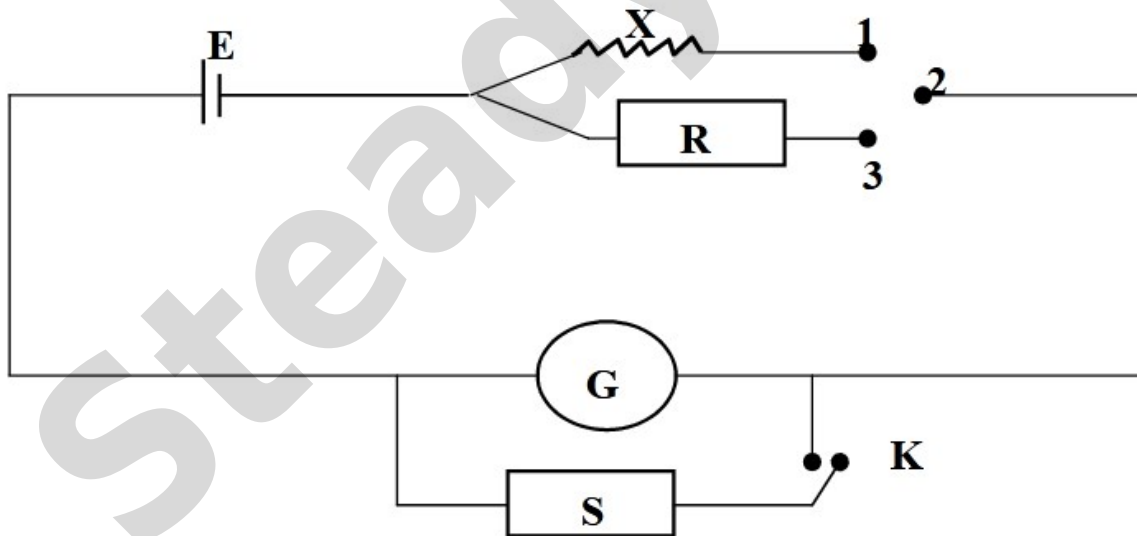

Theory

The connections are made as shown in Fig. below. The key between the terminals 1 and 2 is inserted so as to pass current through the unknown resistance X and the deflection of the galvanometer is noted. The current passing through the galvanometer, I_g , is given by

$$I_g = \frac{E}{R+G} \dots\dots\dots (1)$$

Here E is the e.m.f. of the battery and G is the galvanometer resistance. The key between 1 & 2 are now removed. Some high resistance, R, from the resistance box is introduced and key between the terminals 3 and 2 is inserted. As $R \gg X$, the galvanometer will give larger deflection which may be out of range. Insert the key K and adjust the value of shunt resistance, S, so that deflection in galvanometer is same as it was with X earlier. The current passing through the galvanometer, I_g , is given by

$$I_g = \frac{E}{R + \frac{GS}{G+S}} \times \frac{S}{G+S} \Rightarrow I_g = \frac{ES}{R(G+S) + GS} \dots\dots\dots (2)$$

A current flowing through the galvanometer in two cases is equal, so, from (1) and (2), we have,

$$\frac{E}{X+G} = \frac{ES}{R(G+S) + GS} \Rightarrow X = R \frac{G+S}{S}.$$

Procedure

Make the connections as shown in earlier figure.

- (a) Introduce high resistance from R and then inert plug between 1 & 2 of two way key. Adjust R to get full deflection in the galvanometer. Note this deflection n and value of R.
- (b) Insert plug in key K. Keeping R fixed adjust S so that the deflection in the galvanometer becomes half of the previous deflection, i.e., n/2. Note this deflection and the value of S.
- (c) Repeat steps (2) & (3) for different R.
- (d) Remove plug from 2 & 3, and, insert into terminal between 1 & 2 to bring the unknown resistance X in the circuit. Remove plug in key K. Note down the deflection.
- (e) Remove plug from 1 & 2, and, insert into terminal between 2 & 3. Insert plug in key K. Take out a resistance from high resistance box R. Adjust the value of S so that the deflection is exactly the same as in the previous step.
- (f) Repeat step (e) for different combinations of R & S.

Observation Table

The value of G = 02 K Ω

Sr. No.	Deflection with		Resistance inserted, R (Ω)	Shunt resistance S (Ω)	$X = \left[R \times \frac{G+S}{S} + G \right] \theta_2 / \theta_1 - G$ KΩ	Mean X (KΩ)
	(X)θ ₁	(R)θ ₂				
1						
2						
3						
4						
5						

Result

The value of X isK Ω

Precautions

- 1. A high resistance sensitive galvanometer should be used.
- 2. Plugs of resistance boxes, keys should be tight.

Viva Questions and Answers

Question-1: What is galvanometer?

Answer-1: A device used to detect the presence of current in a circuit.

Question-2: How will you find resistance of a galvanometer?

Answer-2: Resistance of a galvanometer can be found by two methods: Equal deflection method and Half deflection method.

Question-3: Explain substitution method?

Answer-3: In this method current is first passed through resistance and deflection in the galvanometer is noted after this unknown resistance is replaced by resistance R and shunt S , the values of R and S are adjusted in such a manner that galvanometer shows same deflection. The value of unknown resistance is given as: $X = R(G+S)/S$

Question-4: What is the deflection between galvanometer and ammeter?

Answer-4: The resistance of ammeter is higher than that of galvanometer. Further, galvanometer is used to detect the presence of current in the circuit whereas ammeter is used to measure low current in the circuit.

Question-5: What is shunt?

Answer-5: A shunt is a small resistance connected in parallel with galvanometer. It provides a bypass of current through the galvanometer.